

GATE

Prof.G V V sharma

January 29, 2024

- Figure 1 A four-variable Boolean function is realized using 4X1 multiplexers as shown in the figure.

(GATE IN 2018)

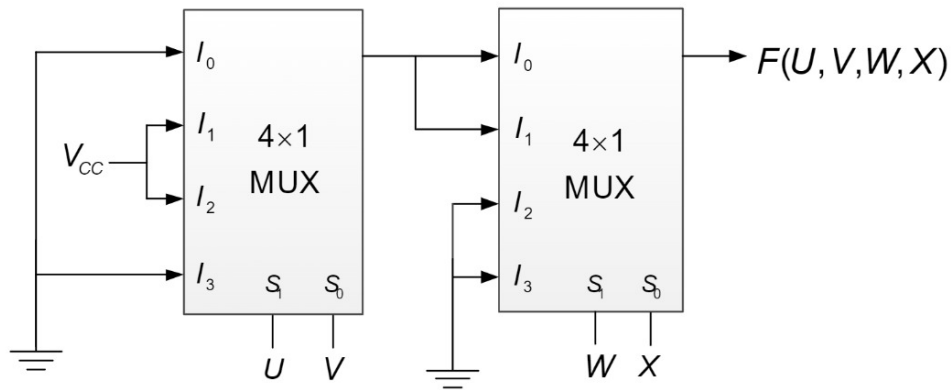


Figure 1: circuit

The minimized expression for $F(U, V, W, X)$ is

- $(UV + \bar{U}\bar{V})\bar{W}$
- $(UV + \bar{U}\bar{V})(\bar{W}\bar{X} + \bar{W}X)$
- $(U\bar{V} + \bar{U}V)\bar{W}$
- $(U\bar{V} + \bar{U}V)(\bar{W}\bar{X} + \bar{W}X)$